

1-masala (RL-zanjir)

$$\tau = L/R$$
$$\tau = 0,40/5 = 0,08 \text{ s}$$

$$I_0 = \varepsilon/R$$
$$I_0 = 20/5 = 4 \text{ A}$$

$$I(t) = I_0 \cdot (1 - e^{-t/\tau})$$

$$t/\tau = 0,20/0,08 = 2,5$$
$$e^{-2,5} \approx 0,082$$

$$I = 4 \cdot (1 - 0,082) = 3,67 \text{ A}$$

$$W = L \cdot I^2/2$$
$$W = 0,40 \cdot (3,67)^2/2 \approx 2,7 \text{ J}$$

2-masala (RL — uzish)

$$\tau = L/R$$
$$\tau = 0,30/6 = 0,05 \text{ s}$$

$$I(t) = I_0 \cdot e^{-t/\tau}$$

$$t/\tau = 0,10/0,05 = 2$$
$$e^{-2} \approx 0,135$$

$$I = 3 \cdot 0,135 = 0,41 \text{ A}$$

$$P = I^2 \cdot R$$
$$P = (0,41)^2 \cdot 6 \approx 1,0 \text{ W}$$

3-masala (RC — zaryadlanish)

$$\tau = R \cdot C$$
$$\tau = 4000 \cdot 0,00025 = 1 \text{ s}$$

$$I_0 = \varepsilon/R$$
$$I_0 = 16/4000 = 0,004 \text{ A} = 4 \text{ mA}$$

$$U(t) = \varepsilon \cdot (1 - e^{-t/\tau})$$

$$t = 2\tau \rightarrow e^{-2} \approx 0,135$$

$$U = 16 \cdot (1 - 0,135) = 13,8 V$$

$$W = C \cdot U^2/2$$

$$W = 0,00025 \cdot (13,8)^2/2 \approx 0,024 J$$

4-masala (RC — razryadlanish)

$$\tau = R \cdot C$$

$$\tau = 2000 \cdot 0,0001 = 0,20 s$$

$$U(t) = U_0 \cdot e^{-t/\tau}$$

$$t/\tau = 0,50/0,20 = 2,5$$

$$e^{-2,5} \approx 0,082$$

$$U \approx 12 \cdot 0,082 \approx 0,98 V$$

$$I = U/R$$

$$I \approx 0,98/2000 = 0,49 mA$$

$$W = C \cdot U^2/2$$

$$W \approx 0,0001 \cdot (0,98)^2/2 \approx 4,8 \cdot 10^{-5} J$$

5-masala (RL va RC)

RL-zanjir:

$$\tau_1 = L/R = 0,50/10 = 0,05 s$$

RC-zanjir:

$$\tau_2 = R \cdot C = 10 \cdot 0,050 = 0,50 s$$

Tezroq jarayon — τ kichik bo'lgan $\rightarrow$ RL

τ teng bo'lishi uchun:

$$\tau = R \cdot C$$

$$C = 0,05/10 = 0,005 F$$

6-masala (o'zgaruvchan tok)

$$U^{ok} = U_0/\sqrt{2}$$

$$U^{ok} \approx 310/1,41 \approx 220 V$$

$$I^{ok} = I_0/\sqrt{2}$$

$$I^{\text{ok}} \approx 10/1,41 \approx 7,1 \text{ A}$$

$$\cos\varphi = \cos 60^\circ = 0,5$$

$$P = U^{\text{ok}} \cdot I^{\text{ok}} \cdot \cos\varphi$$

$$P \approx 220 \cdot 7,1 \cdot 0,5 \approx 780 \text{ W}$$

7-masala (AC + energiya)

$$R = U/I$$

$$R = 220/5 = 44 \Omega$$

$$P = U \cdot I$$

$$P = 220 \cdot 5 = 1100 \text{ W}$$

$$A = P \cdot t$$

$$A = 1100 \cdot 600 = 6,6 \cdot 10^5 \text{ J}$$

8-masala (transformator)

$$U_2 = U_1 \cdot N_2/N_1$$

$$U_2 = 220 \cdot 200/800 = 55 \text{ V}$$

$$I_1 = U_2 \cdot I_2/U_1$$

$$I_1 = 55 \cdot 4/220 = 1 \text{ A}$$

$$P = U_2 \cdot I_2 = 220 \text{ W}$$

9-masala (FOIK)

$$P_2 = \eta \cdot P_1$$

$$P_2 = 0,90 \cdot 1100 = 990 \text{ W}$$

$$I_2 = P_2/U_2$$

$$I_2 = 990/110 = 9 \text{ A}$$

10-masala (energiya)

$$W = L \cdot I^2/2$$

$$W = 0,20 \cdot 25/2 = 2,5 \text{ J}$$

Boshlang'ich maksimal tok = 5 A

$$W = W_c$$

$$L \cdot I^2 = C \cdot U^2$$

$$C = (0,20 \cdot 25)/100 = 0,05 F$$