

1-masala yechimi

To'liq zanjir uchun Om qonuni:

$$I_1 = \varepsilon / (R_1 + r)$$

$$I_2 = \varepsilon / (R_2 + r)$$

Berilgan qiymatlarni qo'yamiz:

$$2 = \varepsilon / (3 + r)$$

$$1 = \varepsilon / (7 + r)$$

Birinchi tenglamadan: $\varepsilon = 2(3 + r) = 6 + 2r$

Ikkinchisidan: $\varepsilon = 1(7 + r) = 7 + r$

Tenglaymiz:

$$6 + 2r = 7 + r$$

$$2r - r = 7 - 6$$

$$r = 1 \Omega$$

Endi ε :

$$\varepsilon = 7 + r = 7 + 1 = 8 V$$

Javob: $\varepsilon = 8 V$, $r = 1 \Omega$.

2-masala yechimi

a) Ketma-ket ulash:

EYuK: $\varepsilon_{um} = \varepsilon + \varepsilon = 9 + 9 = 18 V$

Ichki qarshilik: $r_{um} = r + r = 1 + 1 = 2 \Omega$

Tok:

$$I_{ket} = \varepsilon_{um} / (R + r_{um}) = 18 / (8 + 2) = 18 / 10 = 1,8 A$$

b) Parallel ulash (bir xil manbalar):

EYuK: $\varepsilon_{um} = \varepsilon = 9 V$

Ichki qarshilik: $r_{um} = r / n = 1 / 2 = 0,5 \Omega$

Tok:

$$I_{par} = \varepsilon_{um} / (R + r_{um}) = 9 / (8 + 0,5) = 9 / 8,5 \approx 1,06 A$$

c) Tashqi rezistordagi quvvat:

$$P_{ket} = I_{ket}^2 R \approx (1,8)^2 \cdot 8 \approx 3,24 \cdot 8 \approx 25,9 W$$

$$P_{par} = I_{par}^2 R \approx (1,06)^2 \cdot 8 \approx 1,12 \cdot 8 \approx 9 W$$

Javob: Tok ketma-ket ulashda katta, va tashqi rezistordagi quvvat ham ketma-ket ulashda kattaroq.

3-masala yechimi

a) Nominal rejimda:

$$P_n = U_n^2 / R_{lamp}$$

$$R_{lamp} = U_n^2 / P_n = 12^2 / 24 = 144 / 24 = 6 \Omega$$

b) $U = 9 \text{ V}$ bo'lganda:

$$P = U^2 / R_{lamp} = 9^2 / 6 = 81 / 6 \approx 13,5 \text{ W}$$

Javob: $R_{lamp} = 6 \Omega, P \approx 13,5 \text{ W}$.

4-masala yechimi

a) Ketma-ket zanjir: $R_{um} = R_1 + R_2 = 4 + 6 = 10 \Omega$

Tok:

$$I = U / R_{um} = 20 / 10 = 2 \text{ A}$$

b) Kuchlanishlar:

$$U_1 = I \cdot R_1 = 2 \cdot 4 = 8 \text{ V}$$

$$U_2 = I \cdot R_2 = 2 \cdot 6 = 12 \text{ V}$$

c) Quvvatlar:

$$P_1 = I^2 R_1 = 2^2 \cdot 4 = 4 \cdot 4 = 16 \text{ W}$$

$$P_2 = I^2 R_2 = 4 \cdot 6 = 24 \text{ W}$$

Ko'proq quvvat R_2 da ajraladi $\rightarrow$ u ko'proq qiziydi.

5-masala yechimi

Kirxgofning 1-qonuni:

$$I_{kir} = I_{chiq}$$

$$I_1 + I_2 = I_3 + I_4$$

$$3 + 4 = I_3 + I_4$$

$$7 = I_3 + I_4$$

Berilgan: $I_3 = I_4$

Shuning uchun:

$$\begin{aligned}I_3 + I_3 &= 7 \\2 I_3 &= 7 \\I_3 &= 3,5 A\end{aligned}$$

Demak $I_4 = 3,5 A$.

Javob: $I_3 = 3,5 A, I_4 = 3,5 A$.

6-masala yechimi

Rezistordagi kuchlanish $U = 7,2 V$, tok $I = 0,8 A$.

a) Rezistor qarshiligi:

$$R = U / I = 7,2 / 0,8 = 9 \Omega$$

Ammo shartda tashqi $R = 10 \Omega$ deyilgandi. Demak $7,2 V$ – bu manba uchlaridagi kuchlanish, $0,8 A$ – umumiy tok. Bu holda:

$$I = \varepsilon / (R + r)$$

$U = I R = 0,8 \cdot 10 = 8 V$ bo'lishi kerak edi, lekin $7,2 V$ berilgan — kelishmayapti.

Shuning uchun bu masalada U ni manba uchlarida o'lchangan deb qabul qilamiz va quyidagicha ishlaymiz:

Manba uchlaridagi kuchlanish:

$$U = \varepsilon - I r$$

Boshqa tomondan $U = I R$

Demak:

$$I R = \varepsilon - I r$$

$$I(R + r) = \varepsilon$$

Shuningdek to'liq zanjir uchun ham shu:

$$\varepsilon = I(R + r)$$

Demak $\varepsilon = 0,8(R + r)$. Bizda $R = 10 \Omega$:

$$\varepsilon = 0,8(10 + r)$$

$U = I R = 0,8 \cdot 10 = 8 V$, lekin shartda $7,2 V$ deyilgani uchun, masalani izchil qilish uchun $U = 8 V$ deb olish mantiqan to'g'riroq bo'ladi. Shunda:

$$\varepsilon = U + I r = 8 + 0,8 r$$

Bu teng $\varepsilon = 0,8(10 + r)$ bilan mos:

$$8 + 0,8 r = 8 + 0,8 r \text{ (har doim bajariladi)}$$

Ya'ni bu sonlar juda mos emas tanlangan. Metodik ma'noda to'g'ri variant quyidagicha bo'ladi:

$$U = 8 \text{ V}, I = 0,8 \text{ A}, R = 10 \Omega \rightarrow \varepsilon = I(R + r)$$

Shartga mos bo'lishi uchun r ni maxsus tanlanadi. Keling, fizik ma'noli yechim beramiz:

$$\varepsilon = I(R + r)$$

Faraz qilamiz $U = 8 \text{ V}$ bo'lishi kerak (klassik holat):

$$\varepsilon = 0,8(10 + r)$$

Ichki qarshilikni, masalan, $r = 2 \Omega$ deb olsak:

$$\varepsilon = 0,8 \cdot 12 = 9,6 \text{ V}$$

Bu holda:

$$U = \varepsilon - I r = 9,6 - 0,8 \cdot 2 = 9,6 - 1,6 = 8 \text{ V}$$

Demak sonlar biroz chalkash tanlangan, lekin formulalar:

$$\begin{aligned} \varepsilon &= I(R + r) \\ r &= (\varepsilon - U) / I \end{aligned}$$

ko'rinishda ishlatiladi.

(Real masala tuzishda U , I , R shunday tanlanadi-ki, ε va r aniq chiqsin.)

7-masala yechimi

a) Joule–Lents qonuni:

$$Q = I^2 R t$$

$$t = 4 \text{ minut} = 240 \text{ s}$$

$$Q = 3^2 \cdot 5 \cdot 240 = 9 \cdot 5 \cdot 240 = 45 \cdot 240 = 10800 \text{ J}$$

b) Suvni qizdirish:

$$Q = m c \Delta t$$

$$\Delta t = Q / (m c) = 10800 / (0,5 \cdot 4200)$$

$$0,5 \cdot 4200 = 2100$$

$$\Delta t = 10800 / 2100 \approx 5,14 \text{ } ^\circ\text{C}$$

Javob: $Q \approx 1,08 \cdot 10^4 \text{ J}$, suv harorati taxminan $5 \text{ } ^\circ\text{C}$ ga oshadi.

8-masala yechimi

$R = 3 \Omega$, $R_v = 9 \Omega$ parallel, manba ideal $\varepsilon = 6 \text{ V}$.

a) Parallel tarmoq ekvivalent qarshiligi:

$$1/R_{eq} = 1/R + 1/R_v = 1/3 + 1/9 = 3/9 + 1/9 = 4/9$$

$$R_{eq} = 9/4 = 2,25 \Omega$$

b) Umumiy tok:

$$I = \varepsilon / R_{eq} = 6 / 2,25 \approx 2,67 \text{ A}$$

c) Parallel tarmoqlarda kuchlanish:

$$U_v = \varepsilon = 6 \text{ V} \text{ (ichki qarshilik yo'q, faqat } R_{eq} \text{ bor)}$$

$$\text{Javob: } R_{eq} = 2,25 \Omega, I \approx 2,67 \text{ A}, U_v = 6 \text{ V}.$$

9-masala yechimi

$$I = 4 \text{ A}, R_1 = 2 \Omega, R_2 = 8 \Omega.$$

a) Quvvatlar:

$$P_1 = I^2 R_1 = 4^2 \cdot 2 = 16 \cdot 2 = 32 \text{ W}$$

$$P_2 = I^2 R_2 = 16 \cdot 8 = 128 \text{ W}$$

b) R_2 da quvvat ancha katta, demak R_2 ko'proq qiziydi.

c) Agar R_2 o'rnida sug'urta simi bo'lsa, aynan shu joy avval kuyadi, chunki unda quvvat juda katta ajraladi.

10-masala yechimi

$$R_1 = 6 \Omega, R_2 = 3 \Omega \text{ parallel, } R_3 = 2 \Omega \text{ ketma-ket.}$$

a) Parallel tarmoq:

$$1/R_{par} = 1/6 + 1/3 = 1/6 + 2/6 = 3/6 = 1/2$$

$$R_{par} = 2 \Omega$$

Ketma-ket R_3 bilan:

$$R_{eq} = R_{par} + R_3 = 2 + 2 = 4 \Omega$$

b) Tok:

$$I = \varepsilon / R_{eq} = 10 / 4 = 2,5 \text{ A}$$

c) Ketma-ket ulanishda R3 dan o'tgandan so'ng parallel tarmoqqa keladi, lekin kuchlanishni soddaroq topamiz:

Butun zanjir kuchlanishi 10 V. $R_{eq} = 4 \Omega, I = 2,5 \text{ A}$ — tekshirish: $U = I R_{eq} = 2,5 \cdot 4 = 10 \text{ V}$.

Parallel tarmoqlardagi kuchlanish U_{par} :

$$U_{par} = I \cdot R_{par} = 2,5 \cdot 2 = 5 \text{ V}$$

Javob: $R_{eq} = 4 \Omega, I = 2,5 \text{ A}, U_{par} = 5 \text{ V}$.